
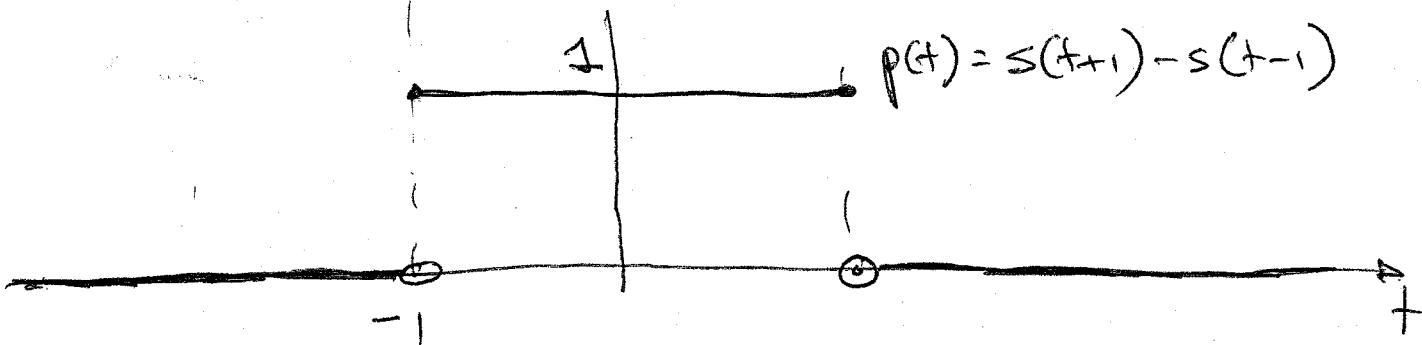
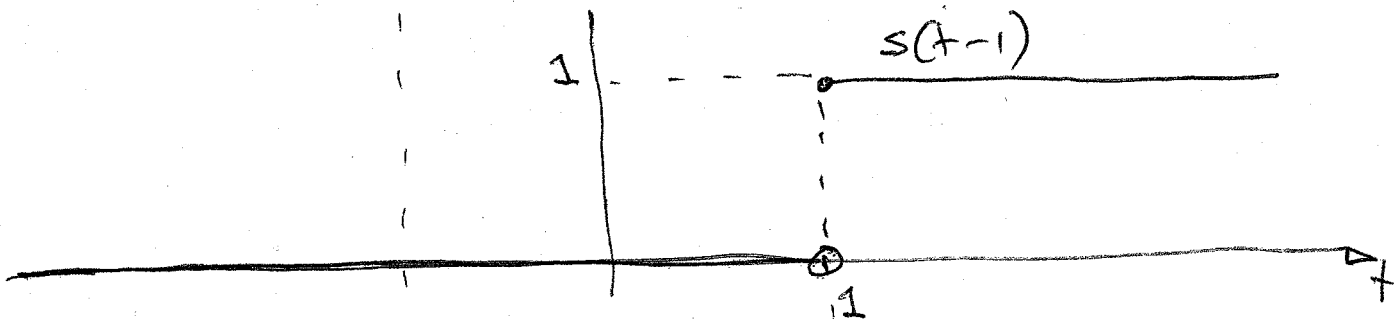
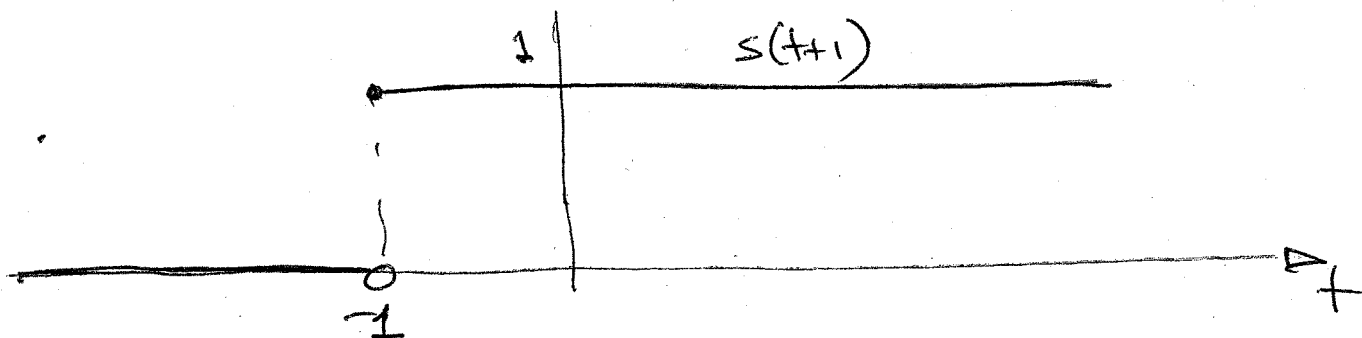


Tutorial #1 Solutions


①

✓
(a)

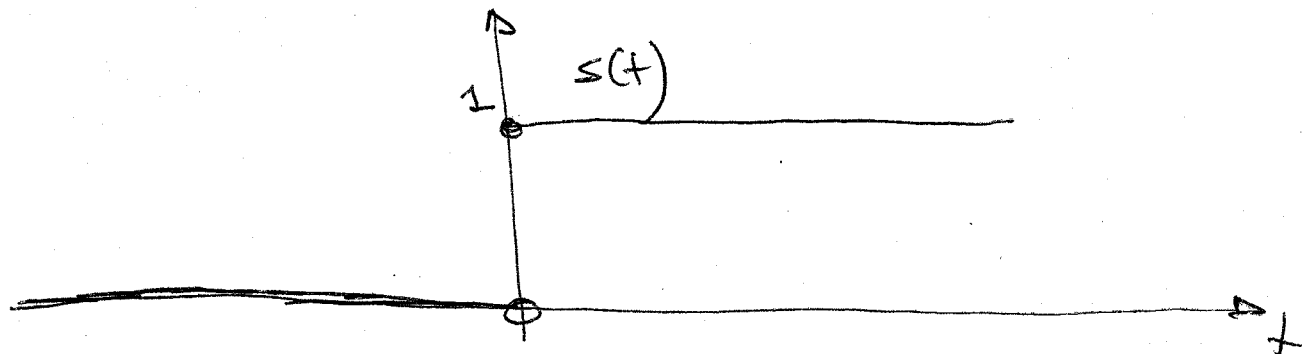


1/ (b) (i)

$$f(t) = p(t/2) + p(t)$$

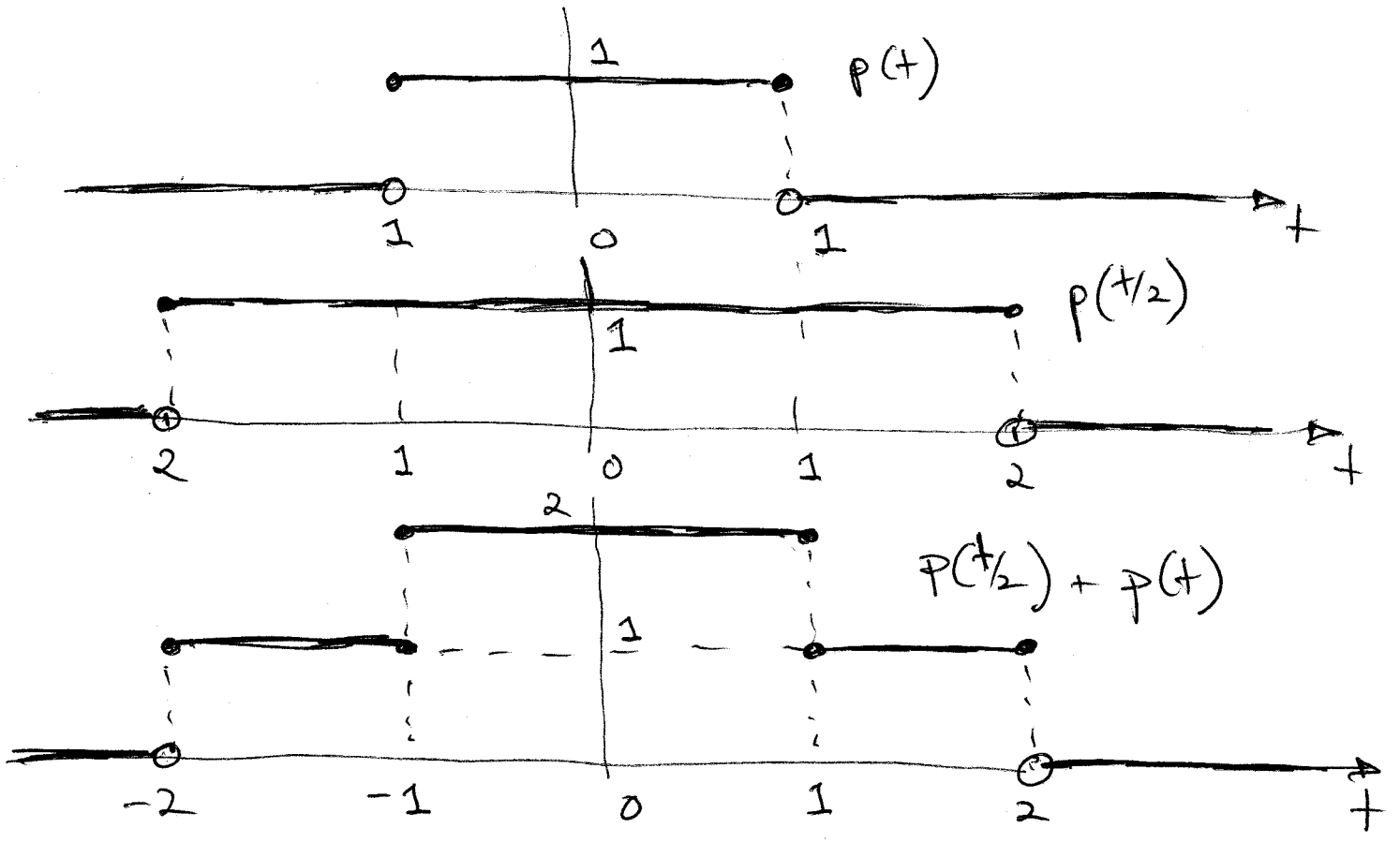


1/ (b) (ii)

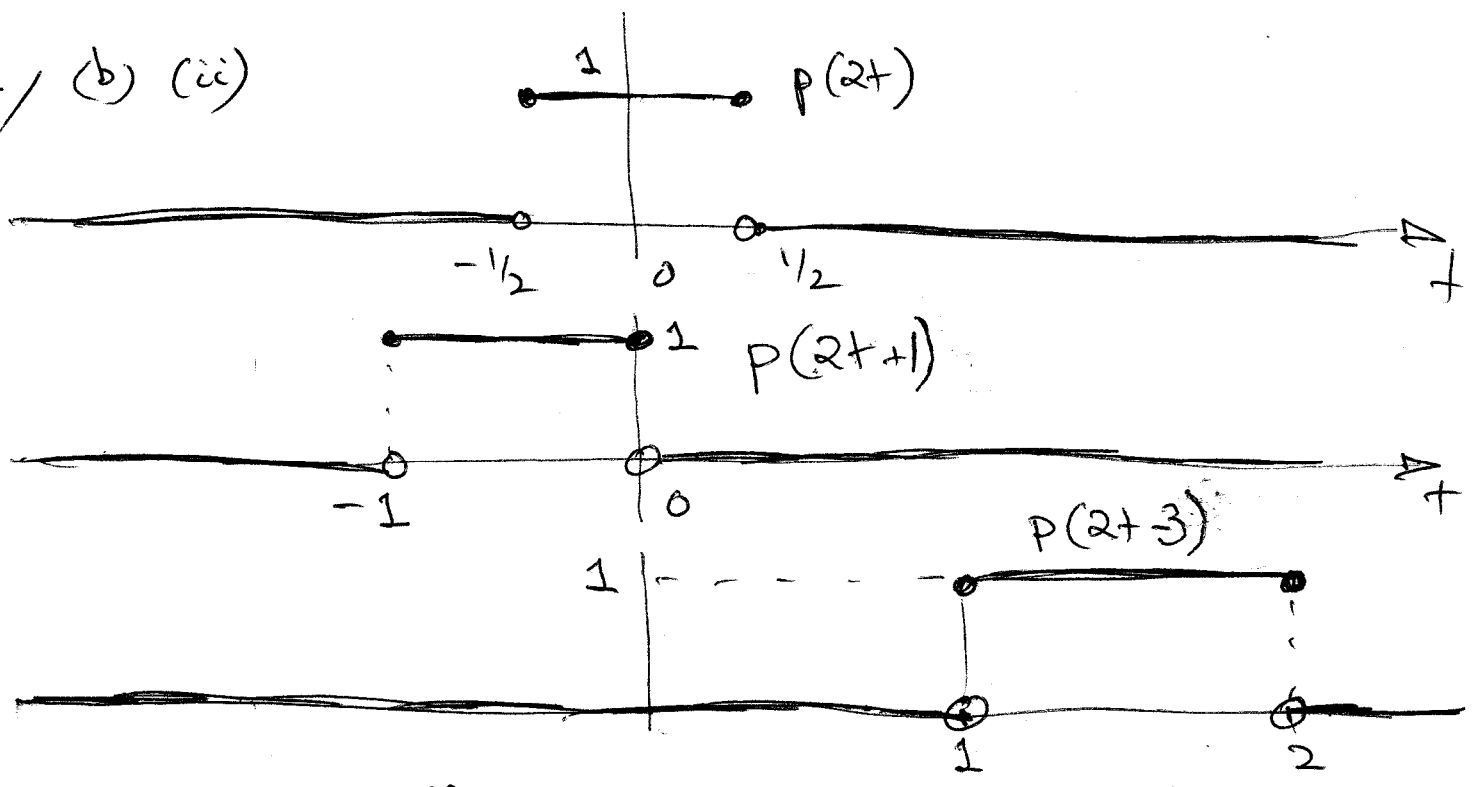


$$g(t) = \sum_{k=-\infty}^{\infty} p(2t + 4k + 1)$$

2/ (c)

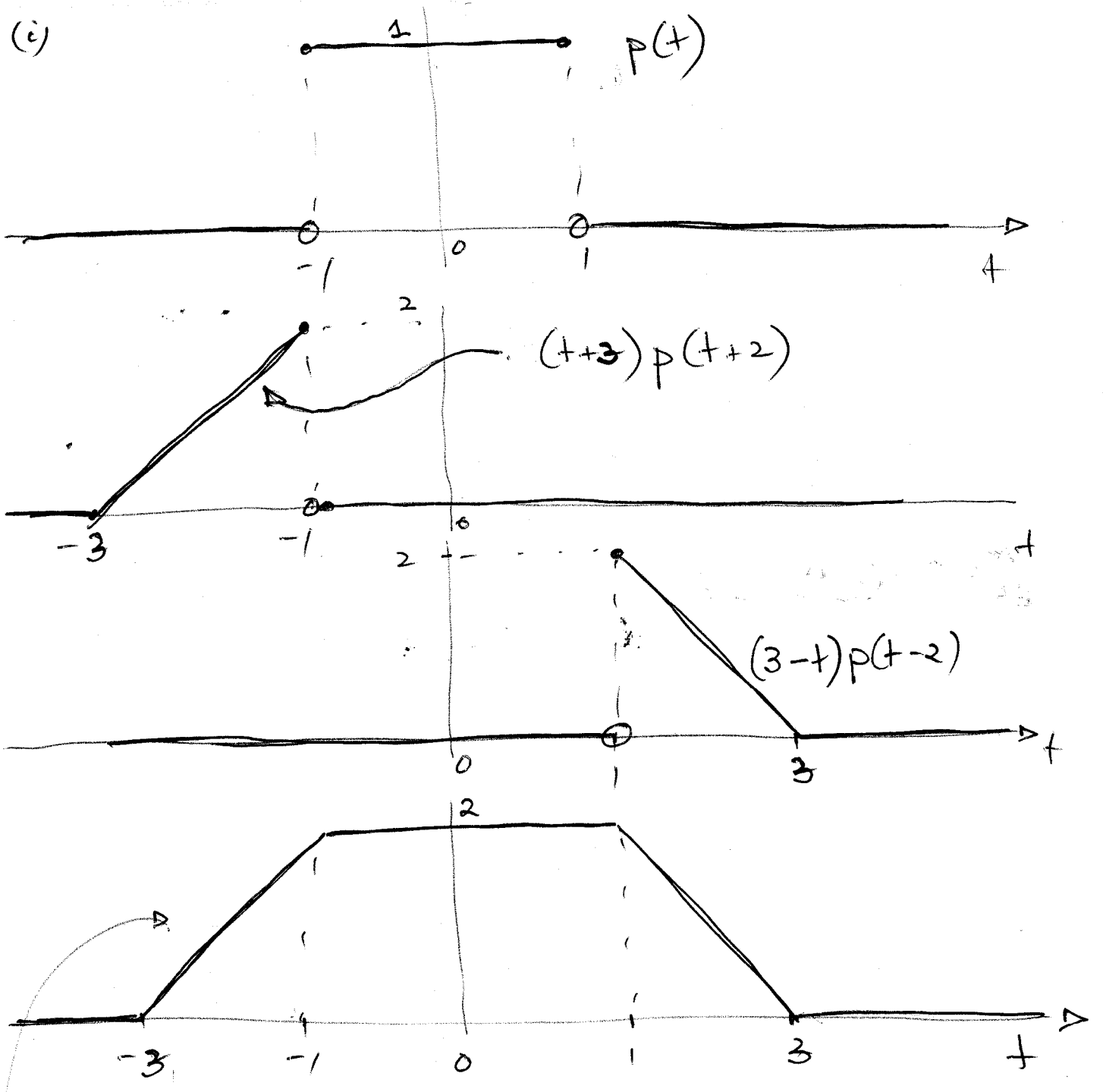


$$2p(t) + (t+3)p(t+2) + (3-t)p(t-2)$$


2/ (a)

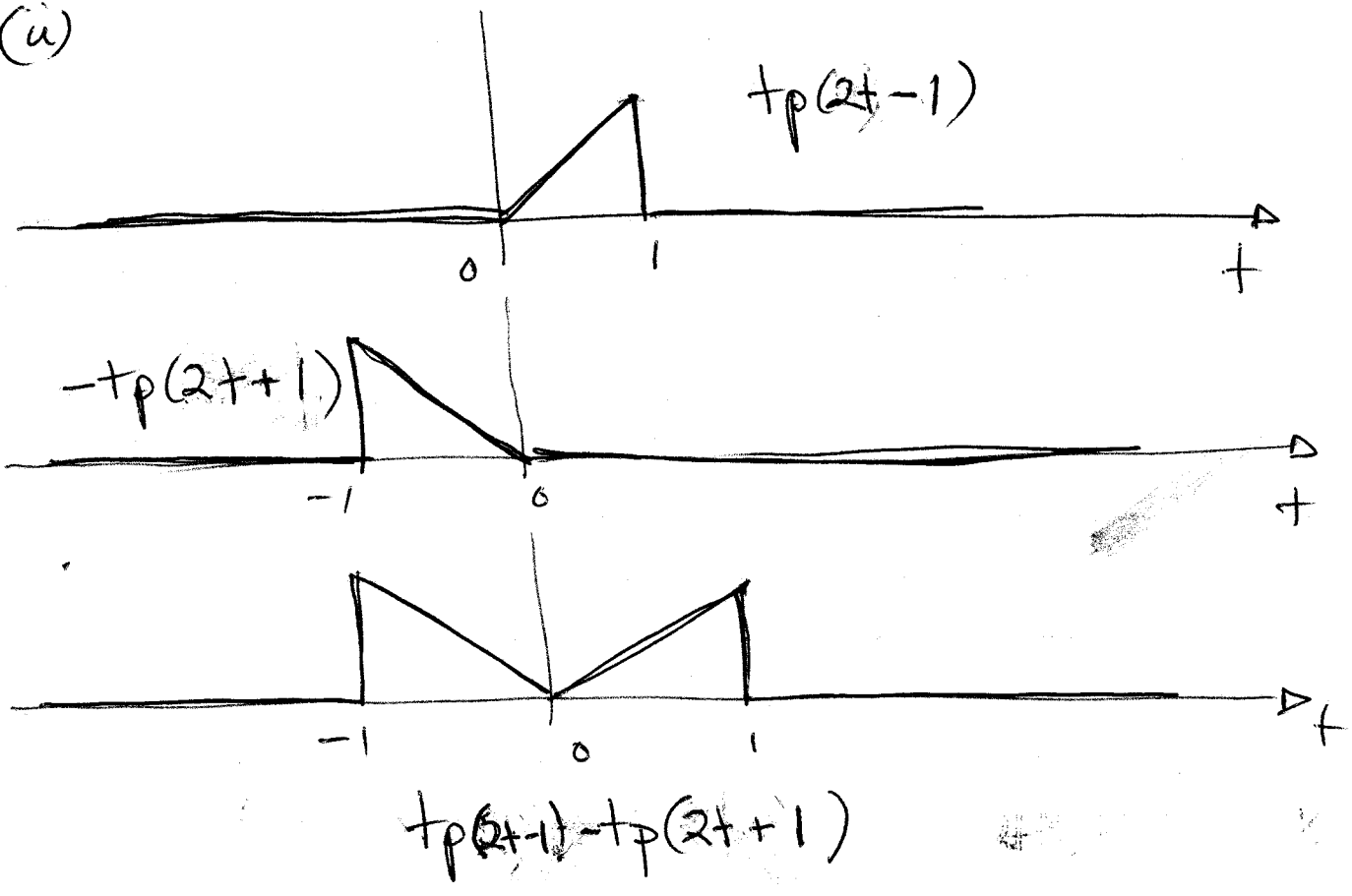


3/ (a)

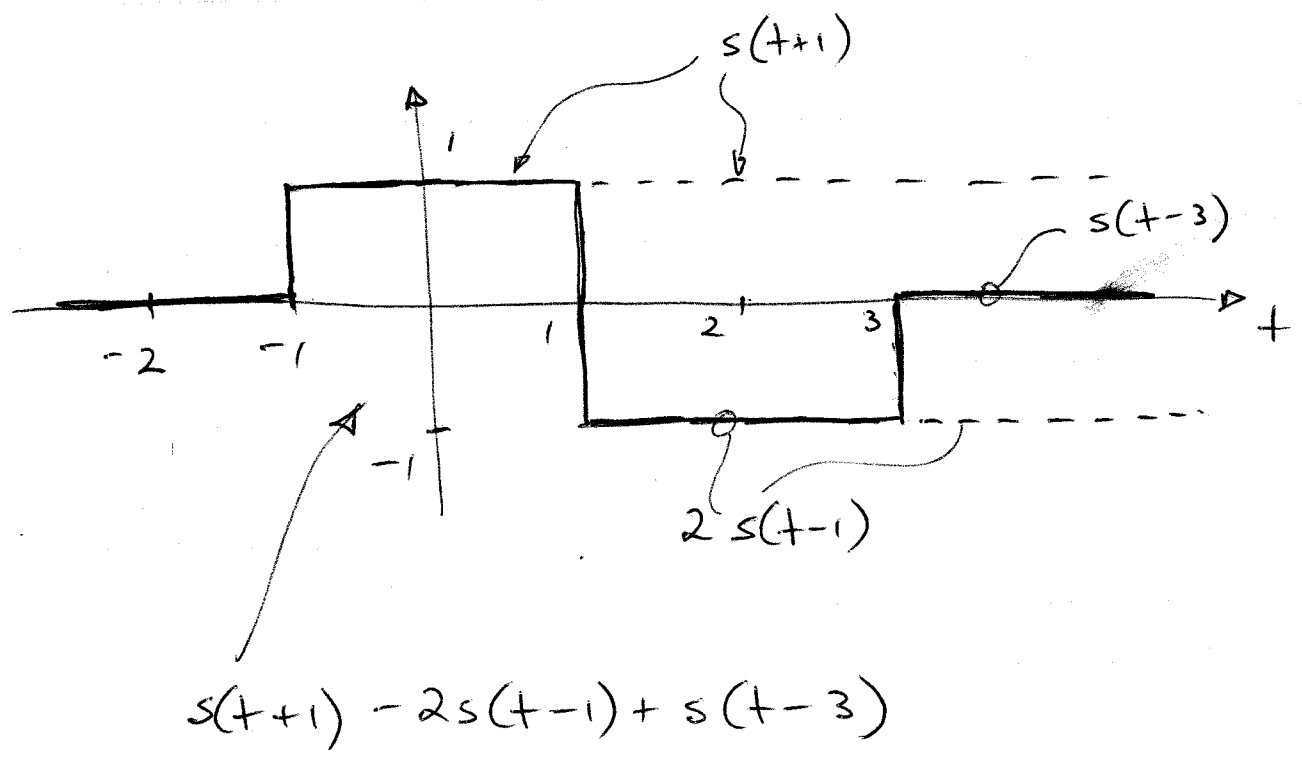


3/
(b)

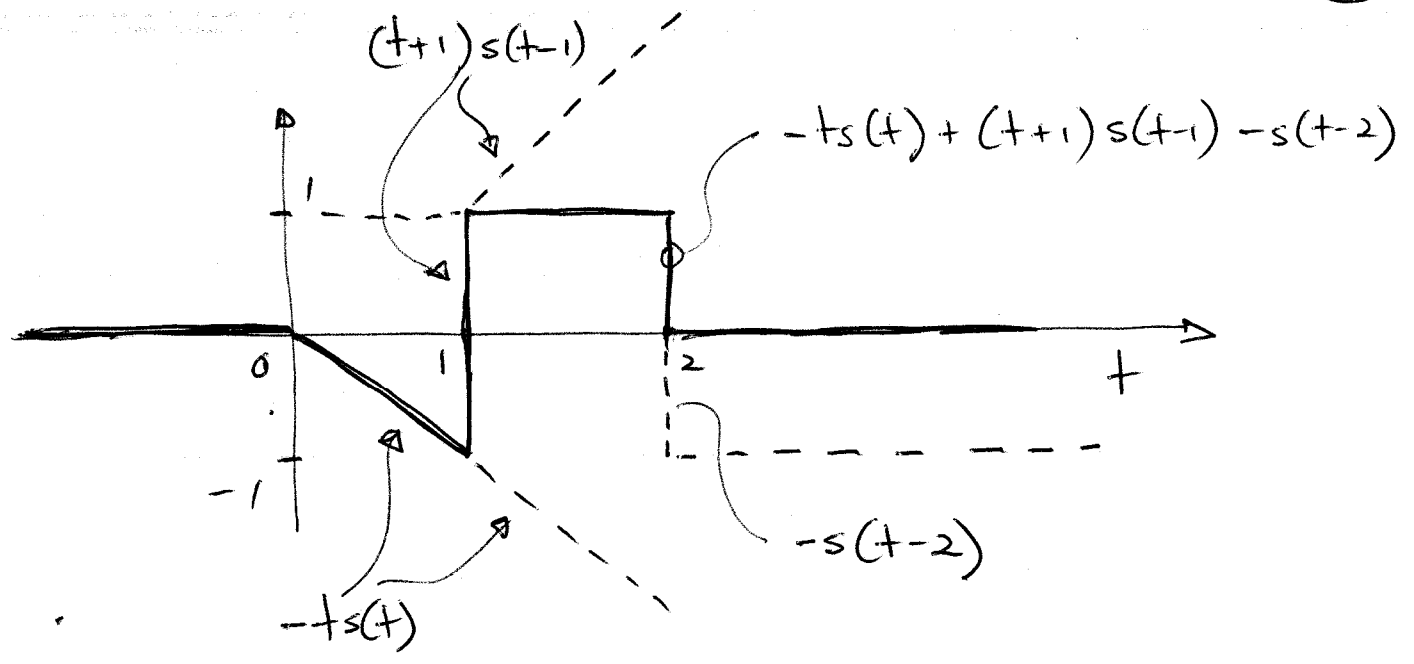

(c)

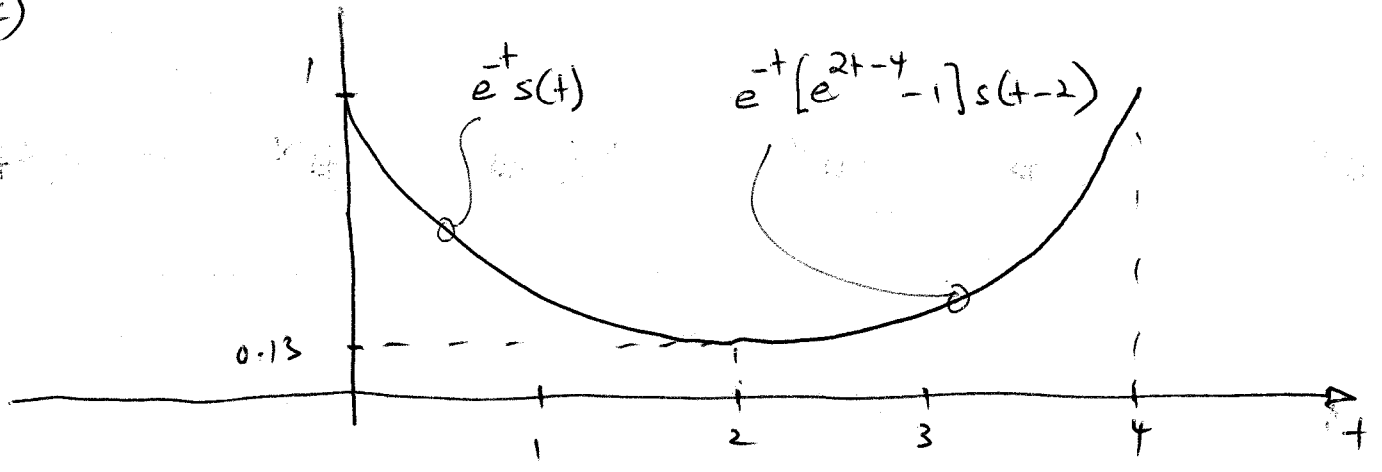


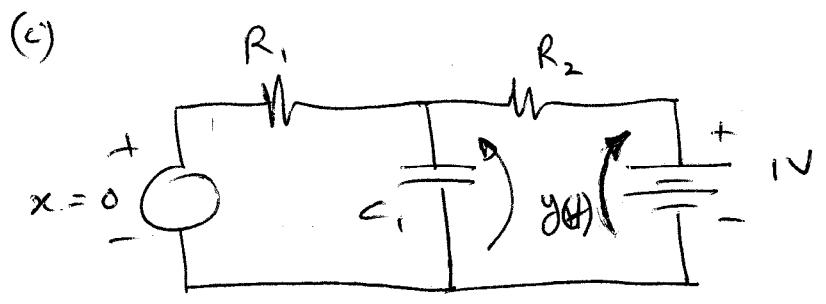4/ For $t < 0$ circuit is (switch is closed)



So $y(0) = v_{C_1} = \frac{1 \cdot R_1}{R_1 + R_2}$ (voltage division)

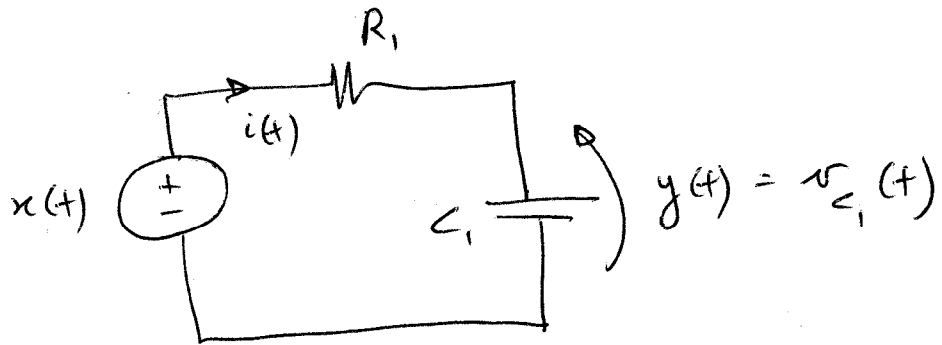4, (ii) For $t \geq 0$ switch is open and circuit becomes



By KVL: $x(t) = R_1 i(t) + y(t)$ (*)

By law of capacitive action

$$i(t) = C_1 \frac{dy(t)}{dt} \quad (**)$$

Substituting (**) in (*) then gives the d.e.

$$x(t) = R_1 C_1 \frac{dy(t)}{dt} + y(t)$$

or

$$\frac{dy(t)}{dt} + \frac{1}{R_1 C_1} y(t) = \frac{1}{R_1 C_1} x(t) \quad (***)$$

(iii) Using integrating factor the d.e. (***) can be rewritten as

$$\frac{d}{dt} \left[y(t) e^{t/R_1 C_1} \right] = \frac{e^{t/R_1 C_1}}{R_1 C_1} x(t)$$

Integrating both sides from $t=0$ to $t=t$

$$y(t)e^{t/R_1} - y(0) = \frac{1}{R_1} \int_0^t e^{\sigma/R_1} x(\sigma) d\sigma$$

However $x(t) = 0$ so the RHS above $= 0$ and therefore

$$y(t) = y(0)e^{-t/R_1} = \frac{R_1}{R_1 + R_2} e^{-t/R_1} \quad ; t \geq 0$$

s/ (a) By KVL

$$x(t) = Ri(t) + y(t)$$

Differentiating both sides $\left(\frac{d}{dt} \right)$ gives

$$\frac{dx(t)}{dt} = R \frac{d}{dt} i(t) + \frac{d}{dt} y(t)$$

By Law for inductor; $i(t) = \frac{1}{L} \int_0^t y(\sigma) d\sigma$ $y(t) = L \frac{d}{dt} i(t)$

Therefore

$$\frac{dx(t)}{dt} = \frac{d}{dt} y(t) + \frac{R}{L} y(t)$$

(8)

(b) Use integrating factor $e^{R/Lt}$ to re-write de. as

$$\frac{d}{dt} \left[e^{R/Lt} y(t) \right] = e^{R/Lt} \frac{d x(t)}{dt}$$

Integrating both sides from 0 to t then gives

$$y(t) e^{R/Lt} - y(0) = \int_0^t e^{R/L\sigma} \frac{d x(\sigma)}{d\sigma} d\sigma$$

Now when $x(t)$ is a unit step, $\frac{d x(t)}{dt} = \delta(t)$

so the RHS above is

$$\int_0^t e^{R/L\sigma} \frac{d x(\sigma)}{d\sigma} d\sigma = \int_0^t e^{R/L\sigma} \delta(\sigma) d\sigma = 1$$

and therefore

$$y(t) = y(0) e^{-R/Lt} + e^{-R/Lt}$$

If $i(t) = 0$ for $t < 0$ then $v_R = 0$ and hence $y(0) = x(0) = 0$ so that

$$y(t) = e^{-R/Lt} ; t > 0$$